

**Part 3**

**Lesson**

**7**

**Controlling a Stepper  
Motor With Remote**

## Overview

In this lesson, you will learn a fun and easy way to control a stepper motor from a distance, using an IR remote control.


The stepper we are using comes with its own driver board making it easy to connect to our UNO.

Since we we wanna not to drive the motor directly from the UNO, we will be using an inexpensive little breadboard power supply, that plugs right into our breadboard and power it with a 9V 1 Amp power supply.


The IR sensor is connected to the UNO directly, since it uses almost no power.

## Component Required:

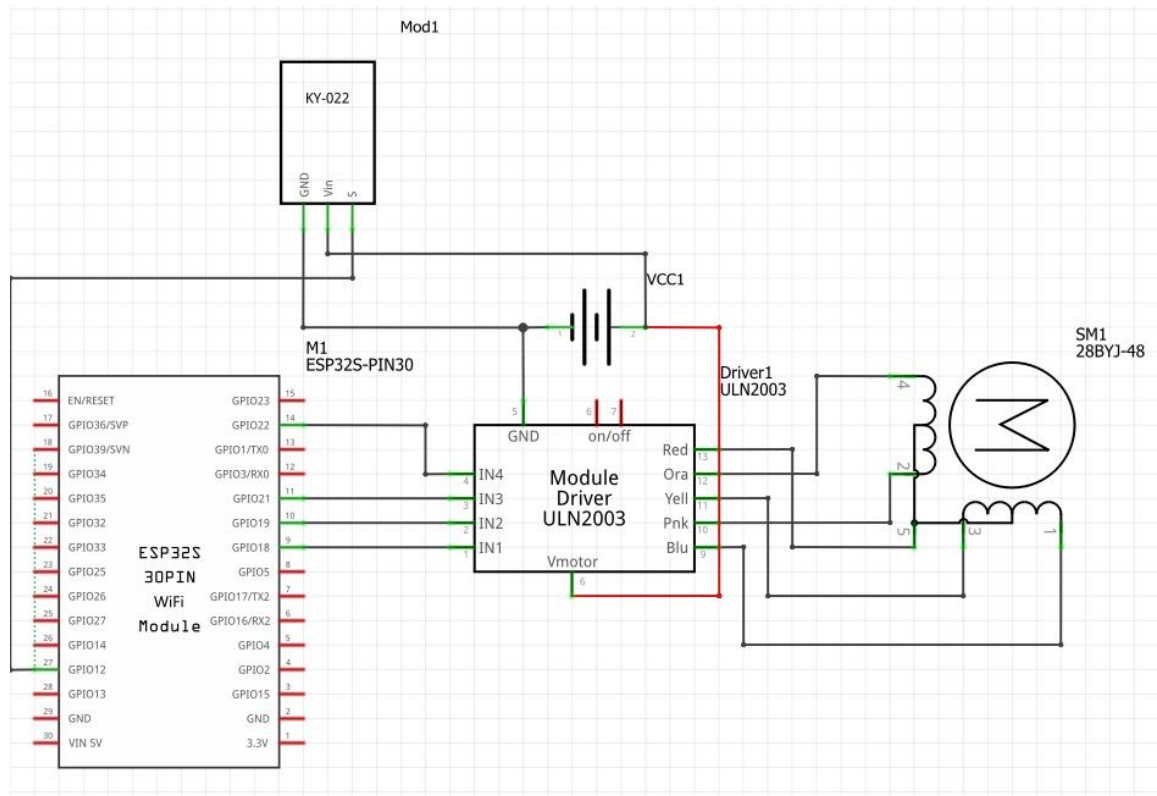- 1) x Elegoo ESP32
- (2) x 400 tie-points breadboard
- (1) x IR receiver module
- (1) x IR remote
- (1) x ULN2003 stepper motor driver module
- (1) x Stepper motor
- (1) x Power supply module
- (1) x 9V1A Adapter
- (9) x F-M wires (Female to Male DuPont wires)
- (1) x M-M wire (Male to Male jumper wire)



**Connection Schematic**

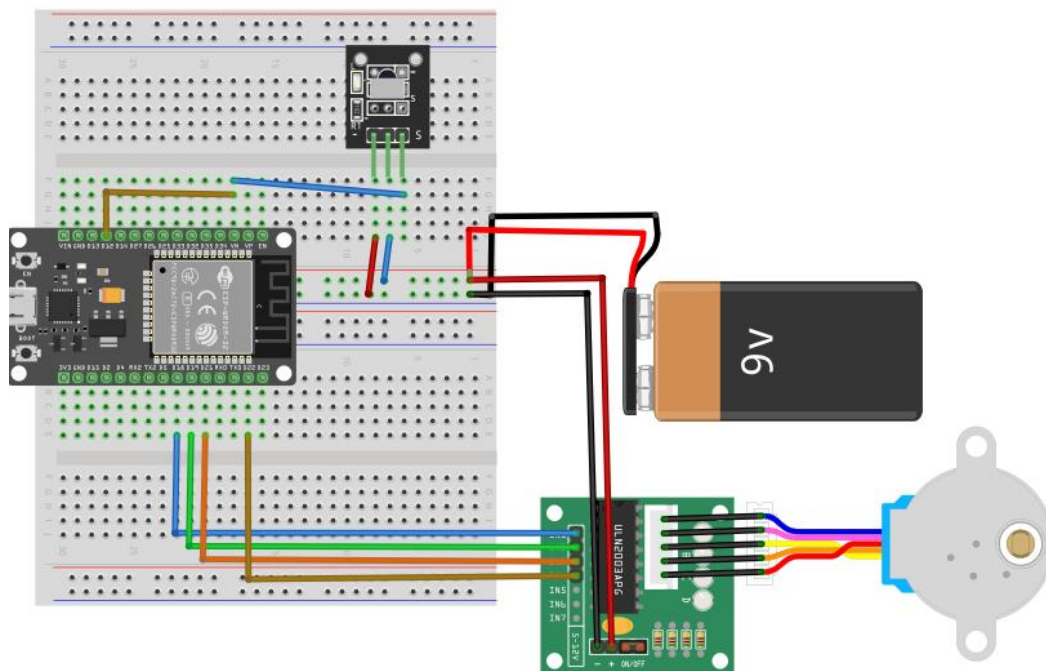

We are using 4 pins to control the Stepper and 1 pin for the IR sensor. GPIO D18-D22 are controlling the Stepper motor and GPIO D5 is receiving the IR information.

**Wiring diagram**

## Code

After wiring, please open program in the code folder **With\_Remote** and click UPLOAD to upload the program. See Lesson 5 of part 1 for details about program uploading if there are any errors.

The code only recognise 2 values from the IR Remote control: positive (+) and negative (-).  
When positive (+) is pressed on the remote the motor will make a full rotation clockwise.  
negative (-) will make a full rotation counter-clockwise.